

Cryptographic Vending Machine

Honours Alpha Team

Luke Malinowski, Brandon Cheng, Cameron Morris

December 11, 2016

Contents

| | | |
|----------|------------------------------------------------|----------|
| 1 | Currency Input IO | 3 |
| 1.1 | Input Details | 3 |
| 1.2 | Output Details | 3 |
| 2 | Operation of the Currency Input Circuit | 3 |
| 2.1 | Initialization | 3 |
| 2.2 | How to Record an Accepted Bill | 4 |
| 2.3 | Maintenance | 4 |
| 3 | Technical Definitions of Terminology | 5 |
| 4 | Change Maker IO | 5 |
| 4.1 | Input Stream Details | 5 |
| 4.2 | Output Stream Details | 5 |
| 5 | Operation of the Change Making Circuit | 6 |
| 5.1 | Initialization | 6 |
| 5.2 | How to Make Change | 6 |
| 5.3 | Maintenance | 7 |

1 Currency Input IO

The purpose of this section is to Provide extra detail on the specification of IO streams and how they interface with other devices.

1.1 Input Details

- **CLK:** The clock signal tells the circuit to add the value of an accepted bill to the value that is currently stored in memory. In a real vending machine, the clock pulse would be generated when the bill reader accepted an inserted bill as valid. We simulate this using a manually operated two-button clock pulse generator.
- **B_{0..5}:** Together these inputs are a binary representation of the value of the bill with B_0 being the least significant bit. In a real vending machine, this number would be generated by the bill reader. We simulate this in our circuit using 6 switches.
- **Selector:** The selector bit switches the ALUs between addition and subtraction while adjusting their C_n bits accordingly. Addition is used for currency input and subtraction is used for vending and making change. The value of this bit is set by the item selection and change making circuits.

1.2 Output Details

- **Dollars In Machine:** There are six D flip flops that store the amount of money currently in the machine. On the board, they are numbered as such where FF represents a 74LS74:

| | | |
|---|----|---|
| 4 | FF | 1 |
| 5 | FF | 2 |
| 6 | FF | 3 |

2 Operation of the Currency Input Circuit

2.1 Initialization

1. After powering on the circuit, reset all of the flip flops to ensure that their value is zero. If this is not done, a user can continuously reboot the machine and collect an amount of change equal to the value of the flip flops as they are powered on. Since they are not guaranteed to initialize to a 1 or 0, skipping this step could lead to losing a lot of money.

2.2 How to Record an Accepted Bill

1. Since we do not have an actual bill reader, we need to set the number of dollars being inserted using switches 1 through 6. These correspond to inputs B_0 through B_5 to the ALU.
2. While the selector bit is set to addition, generate a single clock pulse by pressing the upper button followed by the lower button.
3. On the falling edge, the flip flops will be set to the sum of the input and the value that is already stored in the flip flops.

3 Technical Definitions of Terminology

For the purposes of this circuit the following tables define the values for specific parameters pertaining to this circuit.

| Explicit Name | Canonical Names | Symbol | Value |
|----------------------|-----------------|----------|----------|
| Voltage High | High, H | V_H | (2V-5V) |
| Voltage Low | Low, L | V_L | (0V-.8V) |
| Power Supply Voltage | | V_{cc} | 5V |
| Temperature Range | Min & Max | T_A | (0C-70C) |
| Active State | Active High | | V_H |

4 Change Maker IO

The purpose of this section is to Provide extra detail on the specification of IO streams and how they interface with other devices.

4.1 Input Stream Details

- **Enable Bit:** This bit tells the change maker to start computing and when it is disabled, the circuit will halt no matter what part of the calculation it is in. In addition to this, the enable bit is not shown to the user, it only connects to the vend and bill count circuit.
- **Clock:** The cycling of the clock sequentially makes change. Generally takes 6 clock cycles considering average values for change in machine and number to make change of. This is hidden from user
- **Number to Make Change of:** This value is fed in parallel over the data bus from the vending circuit, and bills in machine circuit. This bus is hidden from user.
- **Counter Reset Switches:** These switches set the bill counters to BILL_MAX which is equal to 15. These are accessible by maintainer.

4.2 Output Stream Details

- **Running:** This bit shows whether or not change is being made. This should halt operation of most other operations. When this is low the

circuit is not doing anything

- **Bill to Dispense:** This is a binary number representing the bill to dispense. This is fed to the bill dispense hardware, but in the prototype this value is displayed on the 4 LEDs.
- **Dispenser Clock:** This sends a clock pulse with the bill to dispense to enqueue the bill current being displayed. This is an LED on the prototype.
- **Counter Low LEDs:** These LEDs indicate when change is low.

5 Operation of the Change Making Circuit

5.1 Initialization

1. Set enable at low
2. Cycle Clock from low to high to low
3. Fill machine with bills to make change
4. Reset change counters, by cycling switches 1,2, and 3 low to high to low

5.2 How to Make Change

1. Feed the value you want to make change of over the data bus
2. Make certain clock and enable are low
3. Set clock to high, then to Low
4. Set enable to high
5. Allow clock to cycle
6. Read output LEDs as bill to dispense and clock for dispenser This prototype emulates support for the bill dispensing machine described in this manual.

5.3 Maintenance

- There are three LED's which mark when their category of bills is empty for that category. The LED's are labeled for their value, and are shown on the specification diagram.
- When the restock change LED's are lit the maintainer must open up the machine and fill up the appropriate bill and then reset its counter by flipping its switch: low to high to low.
- The 10s have a reset switch at 3. The 5s have 2 as their reset switch. The 1s have 1 as their reset switch.
- For clarification to more technical analysis: reset refers to set on the chain of flip flops, but is stated as reset to improve understanding for technicians who lack an electrical or computer engineering background.
- If issues arise where initialization fails try toggling clock while enable is Low.